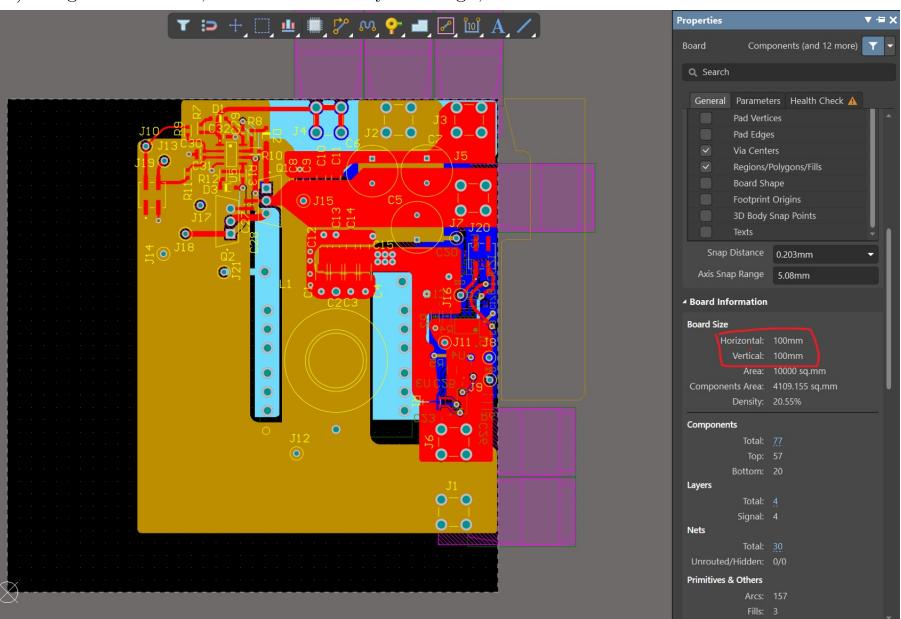


Once you have completed all routing, finalize* your PCB design and ensure the following:

1. Ensure your board is still 100x100 cm, even if you are not using all of the space.
2. Add four non-plated holes (typically in the corners) for standoffs. The standoffs in our parts library have size M3 screws.
3. Write your name in silkscreen somewhere on the top layer of your board. You are welcome to write other (class-appropriate) things in silkscreen, such as a title for your design, or additional labels.




(2).

3mm 0mm • Ro


Shape: Round
Size: 3mm
Tolerance: + N/A - N/A
Length: 0mm
Rotation: 0
Copper Offset (X/Y): 0mm 0mm
Plated:

Hole	Size	Length	Shape	Plated
Pad...	3mm	0mm	• Ro	<input checked="" type="checkbox"/>

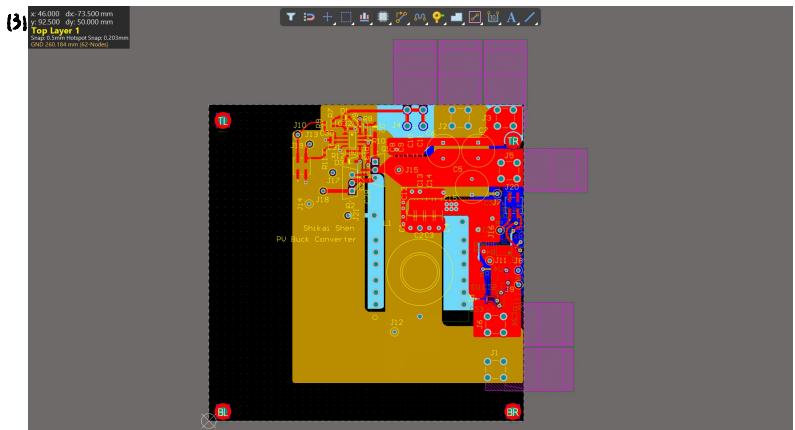

4. Draw a rectangular silkscreen border encircling all parts of your design that will be considered when evaluating your converter's power density. This should include how widely the eligible traces expand on internal layers, including planes. You are welcome to shrink planes to make this area smaller as long as you don't disrupt the performance of your power converter. As a reminder, your converter's power density will be measured based on its box volume (i.e., the volume of the smallest rectangular box that could enclose the whole design) considering all internal power traces, signal traces, planes, and all components besides connectors, test points, and unused parts of the PCB.

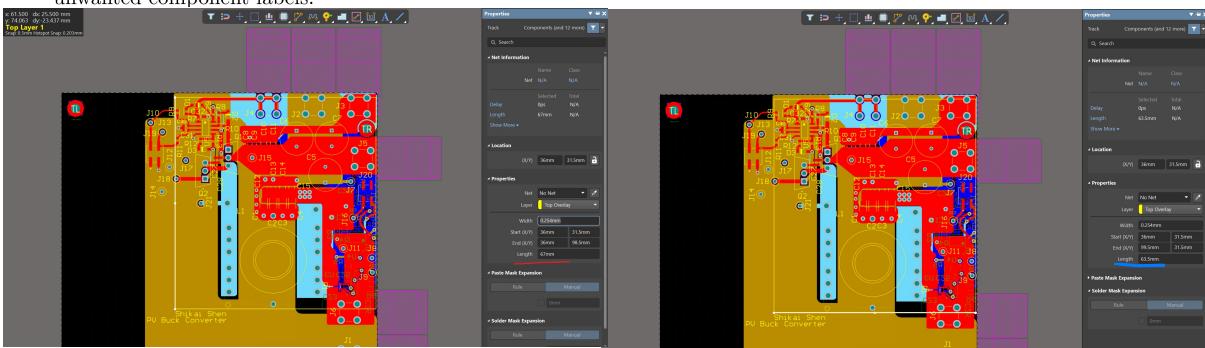5. Ensure all other silkscreen labels are positioned as desired on the PCB. You are not required to keep unwanted component labels.





$$\text{box area} : 67\text{mm} \times 62.5\text{mm} \approx 4254.5\text{mm}^2$$

Design Review Slide Deck


Prepare PowerPoint slides for a PCB design review appointment with course staff. The purpose of these slides is to clearly show important features of your PCB layout with screenshots. For each aspect, you are welcome to use multiple screenshots if necessary, especially if multiple layers are relevant. The slides themselves do not need to be fancy, but the feature of focus should be very clear. You should organize your slides as follows:

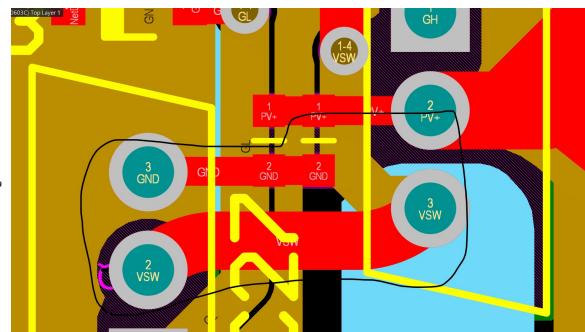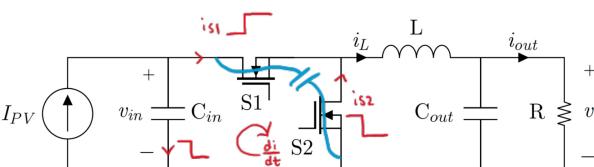1. (213B only) Topology: Show a schematic of your converter topology.
2. Critical Loops: Clearly show with screenshots all critical loops, one by one. This includes all commutation loop(s), gate loop(s), and any other high di/dt loops. For clarity, 213B students should also show each loop of focus on the schematic.
3. Critical Nodes: Clearly show with screenshots all critical nodes, one by one. This includes the switch node(s) and any other high dv/dt nodes. You should include the traces surrounding high dv/dt nodes in your screenshots to show the distance and/or shield between them. For clarity, 213B students should also show each node of focus on the schematic.



commutation loops: [high $\frac{di}{dt}$]



Gate Loops [high $\frac{di}{dt}$]

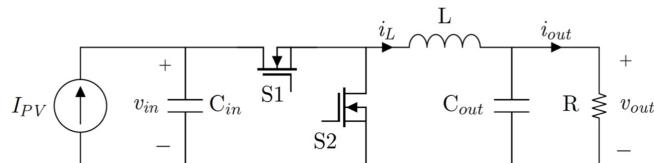



gate drive IC

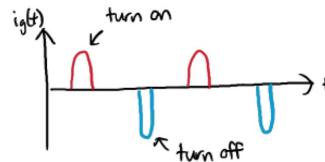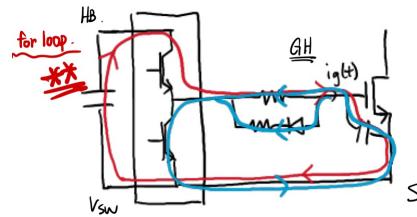

Gate High Loop: $G_H \rightarrow V_{SW} \xrightarrow{BJT} \text{Gate IC}$

Gate IC

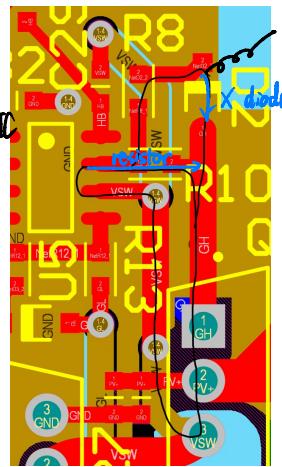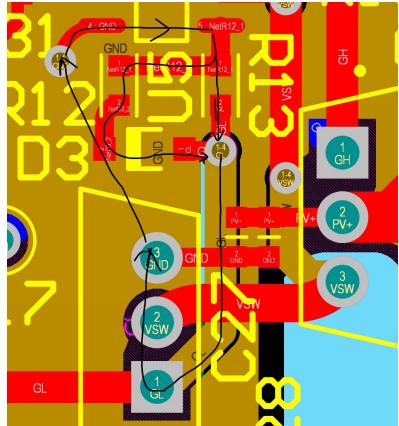
Gate Low Loop: $LO \rightarrow GL \rightarrow GND$



High $\frac{di}{dt}$ loops: commutation, gate high, gate low



3. Critical Nodes: Clearly show with screenshots all critical nodes, one by one. This includes the switch node(s) and any other high dv/dt nodes. You should include the traces surrounding high dv/dt nodes in your screenshots to show the distance and/or shield between them. For clarity, 213B students should also show each node of focus on the schematic.

$\text{high } \frac{dv}{dt}: V_{SW}$

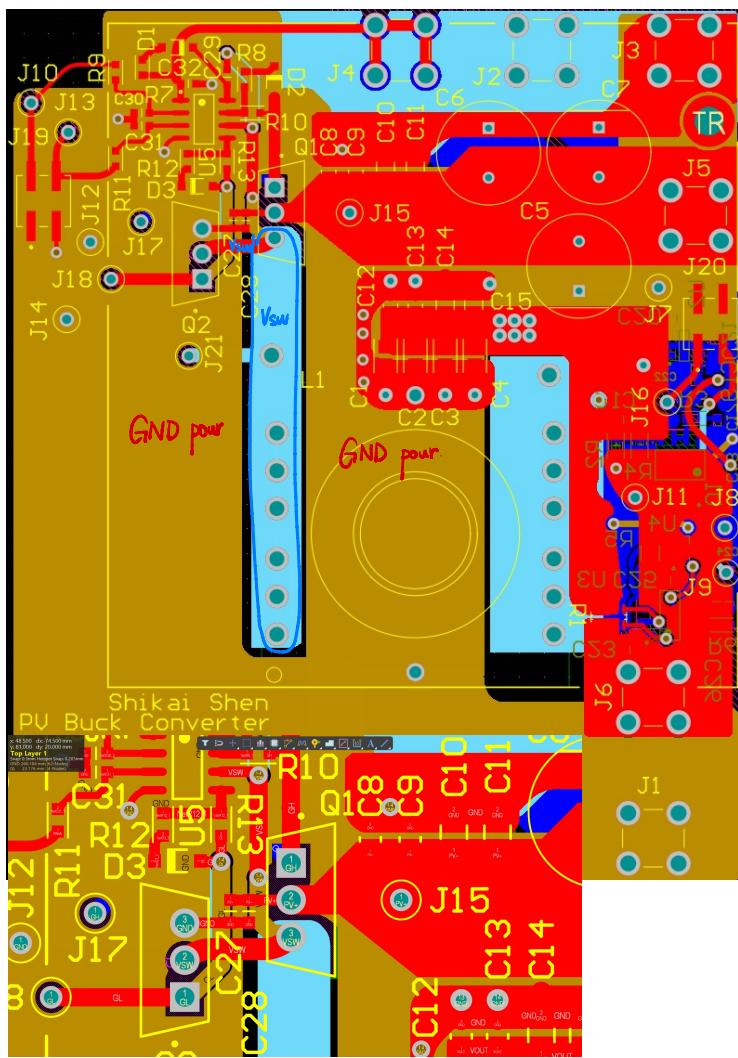


4. Power Stage Current Loops: Show screenshots of all power stage current loops, one by one. Show both the dc and ac current paths for each. For clarity, 213B students should also show each loop of focus on the schematic.
5. Analog Circuit Placement and Routing: Show screenshot(s) of how you have placed and routed analog circuits (e.g., sensing) to minimize interference and ensure minimal differences in ground potential. This includes showing the distance of such components from high di/dt loops and high dv/dt nodes, unless you are using shielding. This also includes showing the power rails and ground connections for these circuits.
6. Digital Circuit Placement and Routing: Show screenshot(s) of how you have placed and routed digital circuits (e.g., gate drive). This also includes showing the power rails and ground connections for these circuits.


power stage current returns:

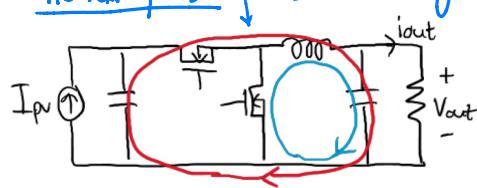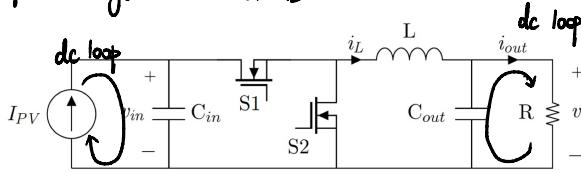


AC loop:

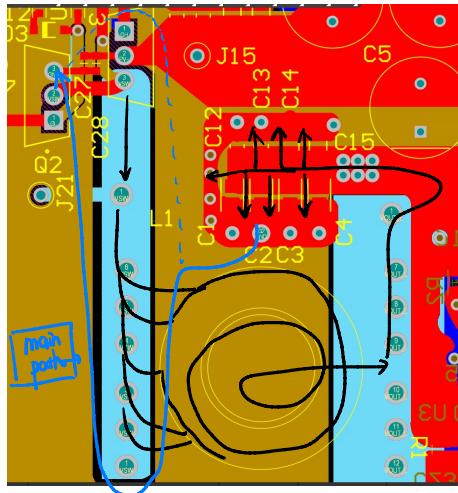

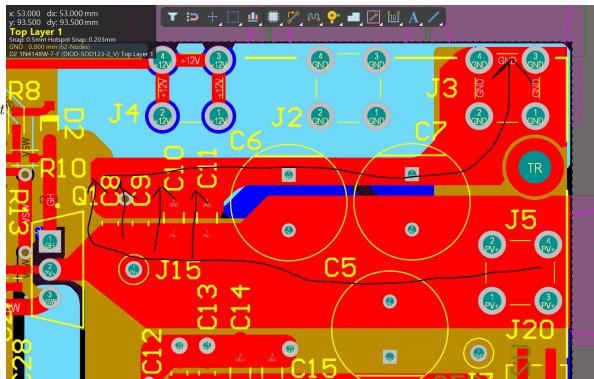DC loops: (source) with large loop area ↓ minimize ESR



DC loop (load) ← minimize ESR

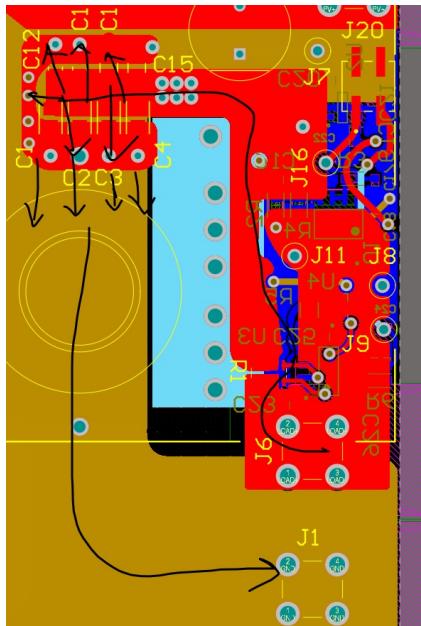


5. Analog Circuit Placement and Routing: Show screenshot(s) of how you have placed and routed analog circuits (e.g., sensing) to minimize interference and ensure minimal differences in ground potential. This includes showing the distance of such components from high di/dt loops and high dv/dt nodes, unless you are using shielding. This also includes showing the power rails and ground connections for these circuits.

6. Digital Circuit Placement and Routing: Show screenshot(s) of how you have placed and routed digital circuits (e.g., gate drive). This also includes showing the power rails and ground connections for these circuits.


Sensing circuit:

Gate IC

high di/dt

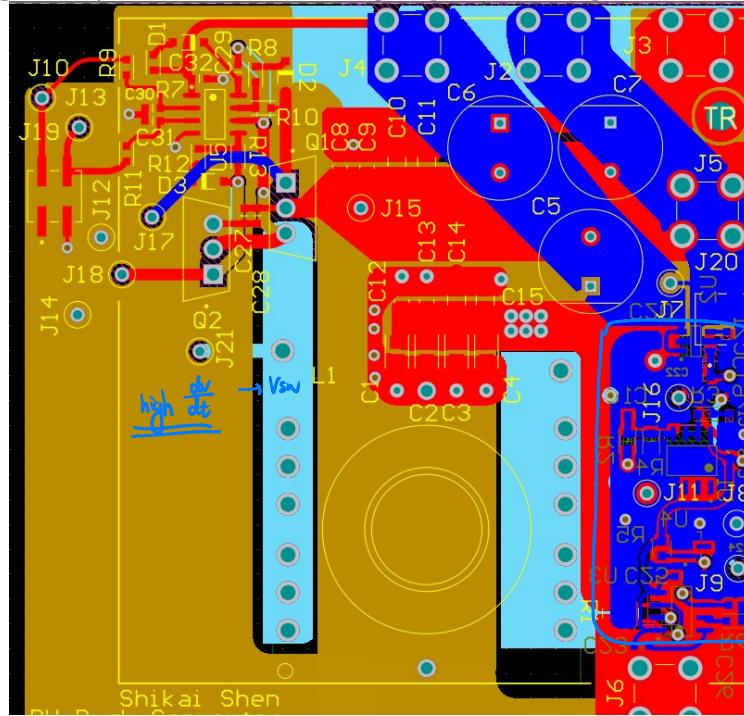


power rails:

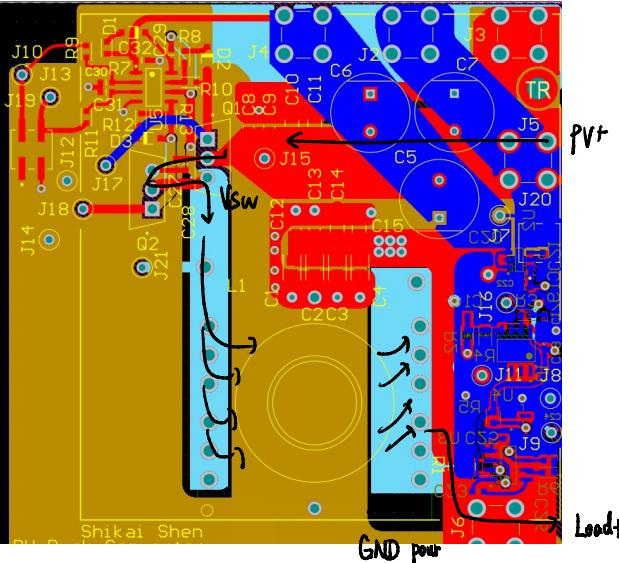


GND connections.


12V 12V's GND Pvt's GND

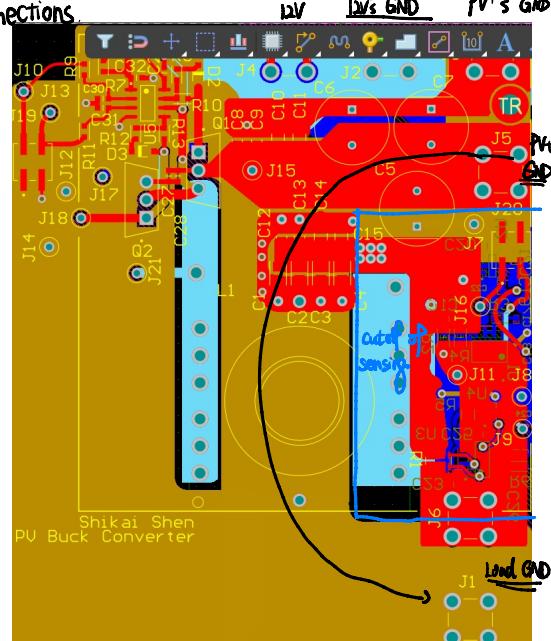

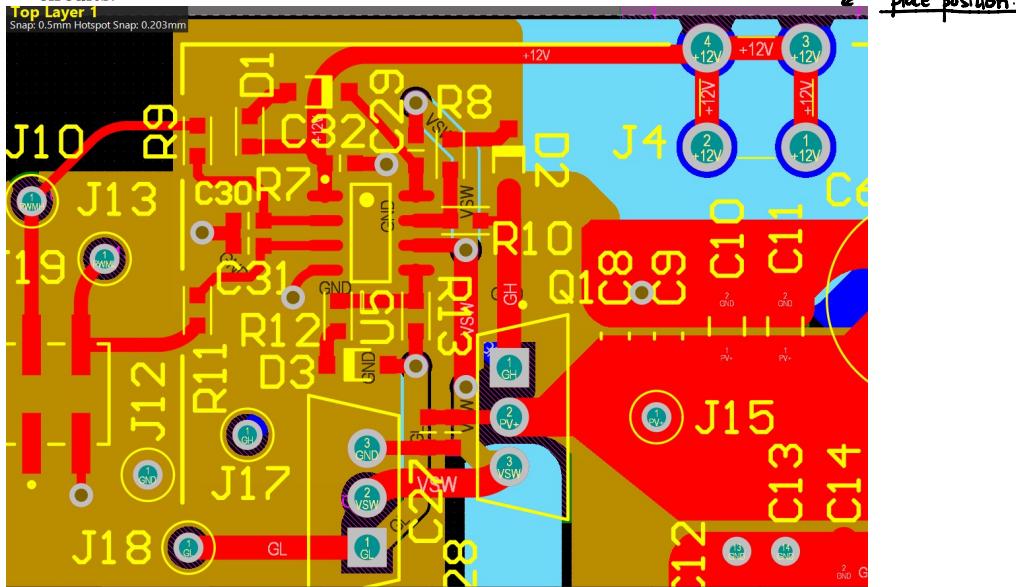6. Digital Circuit Placement and Routing: Show screenshot(s) of how you have placed and routed digital circuits (e.g., gate drive). This also includes showing the power rails and ground connections for these circuits.





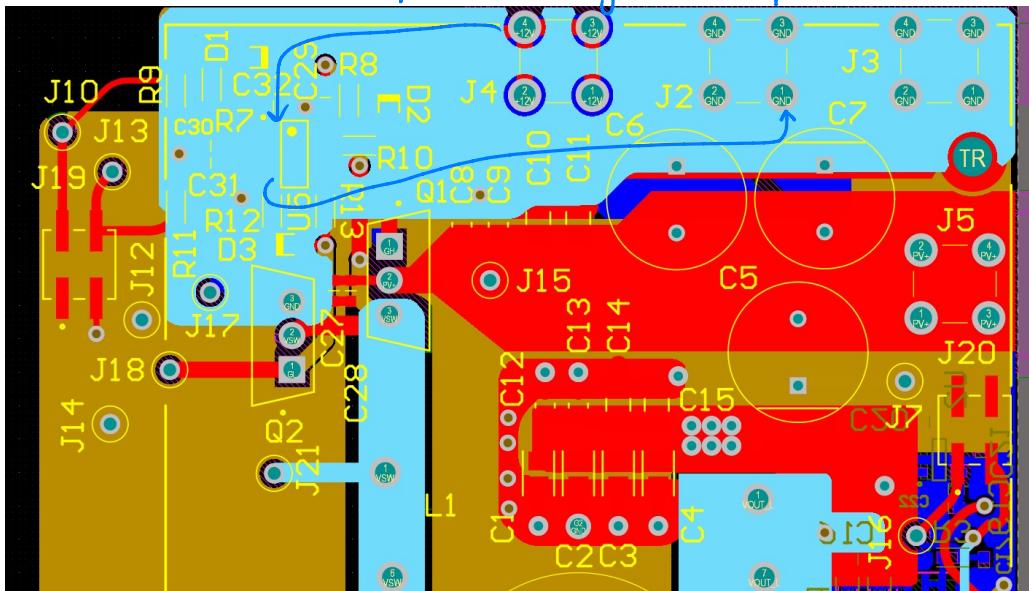
power rails and ground returns of Gate Driver.




7. Test Points: Provide a list of all nets for which you have included test points for probing voltage and loops for probing current. For clarity, 213B students should also show these nets on the schematic.
8. Silkscreen: Show a screenshot with your silkscreen layer and all four copper layers visible, to show that your silkscreen rectangle encloses all relevant traces and planes for power density. Also show that your name is written on the PCB in silkscreen.

(7). PWMH, PWML, GH, GL, VSW, GND

VOUT_ADC, IOUT_SENSE, LOAD+

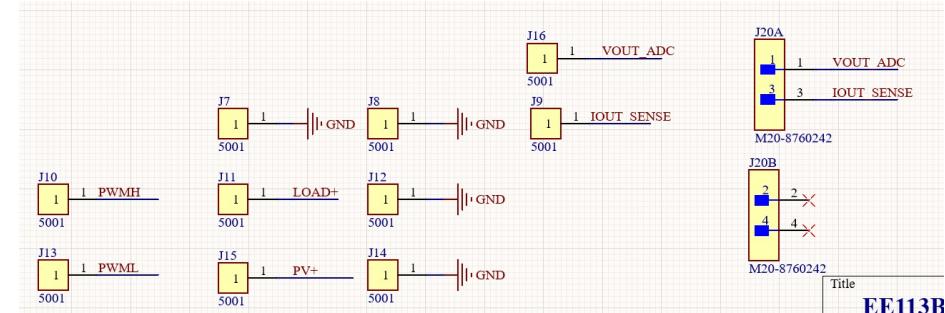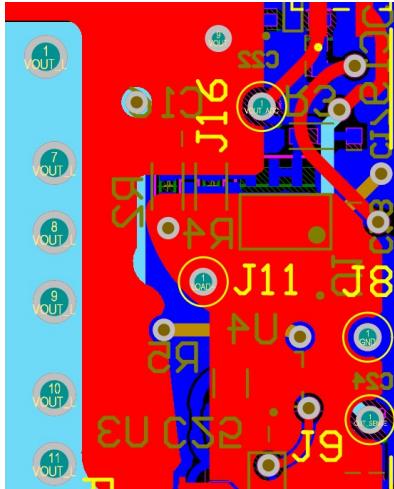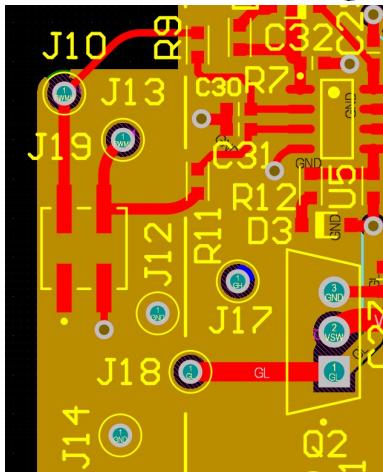

EE113B

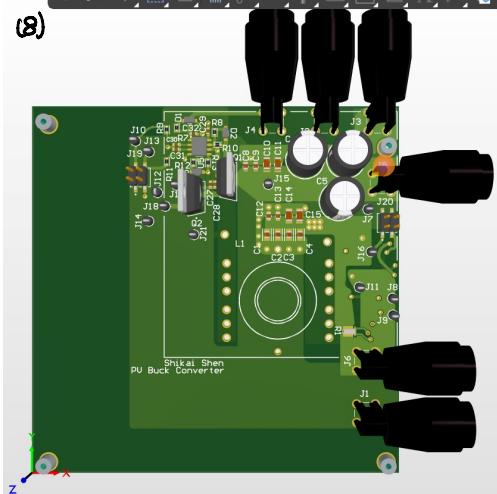

Bill of Materials

Rather than providing a conventional Bill of Materials (BOM), open the BOM spreadsheet linked under this module on bCourses and locate the column with your name. In your column, enter the quantity of each part you will need for one build of your board (not including extra parts). For parts you do not plan to use, enter '0'. Make sure all parts on your PCB schematic are listed on this spreadsheet; this is the spreadsheet course staff will use to determine how many additional parts will need to be ordered. DO NOT modify any column but your own.

EE 213B: Enter parts not currently in our library under the "New Parts" heading at the bottom of the spreadsheet, and provide the part number, Digikey/Mouser link, and cost for a small quantity.

Assignment Feedback (Required)

How much dedicated time did you spend on this pre-lab? Add this at the end of your design review slides.

Submit a PDF of your design review slides to Gradescope.

10μF 0805: 4

470μF electrolytic: 3

22μF 0805: 4

→ 10μF 1206

4.7μF 1206: 4

2.2μF 0603: 2+1=3

330pF 0603: 2

1μF 0603: 1+1=2

1μF 0603: 1+1+1+1=4

10000pF 0603: 1+1=2

0.1μF 0603: 1+1+1=3

10pF 0603: 1

Time: 2.5 hours.

2.5m 0612: 1

1R 0603: 1+2+2=5

10R 0603: 2

2.94kR 0603: 1

120R 0603: 1+1=2

470kR 0603: 1

47kR 0603: 1

A	B	C	D	E	F	G
Name	Part No	Link	Cost [S]	Shen Shikai Quantity	Cost [S/board]	Link
3 PARTS: CONNECTORS LIBRARY						
Heighway connectors (10 pos)	61001011121	https://www.digikey.com/en/products/filter/connector/10-pin-connectors/10-pin-heighway-connectors?k=61001011121	0.00	0	0	
Heighway connectors (4 pos)	61001078642	https://www.digikey.com/en/products/filter/connector/4-pin-connectors/4-pin-heighway-connectors?k=61001078642	0.38	2	0.76	
Test point	5001	https://www.digikey.com/en/products/filter/test-point/1-test-point?k=5001	0.38	13	4.94	
Banana jack, blk	CT3151SP-0	https://www.mouser.com/ProductDetail/Connex/CT3151SP-0	2.45	3	7.35	
Banana jack, red	CT3151-2	https://www.mouser.com/ProductDetail/Connex/CT3151-2	2.45	3	7.35	
10 PARTS: IC LIBRARY						
Half bridge gate driver	LTM1090MAXNOPB	https://www.digikey.com/en/products/filter/ic/half-bridge-gate-drivers/ltm1090maxnopb?k=LTM1090MAXNOPB	1.03	1	1.03	
LM358N	LM358N	https://www.digikey.com/en/products/filter/ic/op-amps/low-power-op-amps/lm358n?k=LM358N	0.44	1	0.44	
Current sense amplifier	LT1995CS-50	https://www.digikey.com/en/products/filter/ic/current-sense-amplifiers/lt1995cs-50?k=LT1995CS-50	6.25	1	6.25	
Voltage reference - 1.25 V	ADR12161ARTZ-REEL7	https://www.digikey.com/en/products/filter/ic/voltage-reference/adr12161artz-reel7?k=ADR12161ARTZ-REEL7	2.28	1	2.28	
Low side gate driver	UCC4227DVR	https://www.digikey.com/en/products/filter/ic/gate-drivers/ucc4227dvr?k=UCC4227DVR	0.83	0	0	
Digital isolator	ISO6720FBDR	https://www.digikey.com/en/products/filter/ic/digital-isolators/iso6720fbdr?k=ISO6720FBDR	1.54	0	0	
Voltage regulator - 3.3 V	LD111ADT33TR	https://www.digikey.com/en/products/filter/ic/voltage-regulators/ld111adt33tr?k=LD111ADT33TR	0.71	0	0	
10 LDO	LP2985-500VBR	https://www.digikey.com/en/products/filter/ic/life-partic平/lp2985-500vbr?k=LP2985-500VBR	0.55	1	0.55	
20 PARTS: SWITCH LIBRARY						
LED	TLM1050A-0308	https://www.digikey.com/en/products/filter/light-emitting-diodes/tlm1050a-0308?k=TLM1050A-0308	0.45	0	0	
Diode	1N1168-7.7F	https://www.digikey.com/en/products/filter/diode/1n1168-7.7f?k=1N1168-7.7F	0.11	3	0.33	
TO-220 55V 29A	IRF234NPF	https://www.digikey.com/en/products/filter/transistor/irf234npf?k=IRF234NPF	0.92	0	0	
TO-220 55V 47A	IRL124NPFR	https://www.digikey.com/en/products/filter/transistor/irl124npfr?k=IRL124NPFR	1.28	0	0	
TO-220 55V 64A	IRF240NPFR	https://www.digikey.com/en/products/filter/transistor/irf240npfr?k=IRF240NPFR	1.27	0	0	
TO-220 55V 89A	IRL370NPBF	https://www.digikey.com/en/products/filter/transistor/irl370npbf?k=IRL370NPBF	1.85	2	3.7	
TO-220 heat sink	50730000000000000000	https://www.digikey.com/en/products/filter/heat-sink/50730000000000000000	0.3	2	0.6	
TO-220 55V 12A	QSD100-05-05	https://www.digikey.com/en/products/filter/transistor/qsd100-05-05?k=QSD100-05-05	0.43	2	0.86	
MLPAK33-25 V32A	PWN1172-25QLJ	https://www.digikey.com/en/products/filter/programmable-power-supply/mlpak33-25-v32a/pwn1172-25qlj?k=MLPAK33-25%20V32A	0.59	0	0	
MLPAK33-25 V65A	PWN16F2-25QLJ	https://www.digikey.com/en/products/filter/programmable-power-supply/mlpak33-25-v65a/pwn16f2-25qlj?k=MLPAK33-25%20V65A	0.58	0	0	
32 PARTS: INDUCTOR LIBRARY						
RM 8 cores (2 piece set)	RM8-3C95	https://www.digikey.com/en/products/filter/inductor/rm8-3c95?k=RM8-3C95	2.32	0	0	
RM 10 cores (2 piece set)	RM10-3C95	https://www.digikey.com/en/products/filter/inductor/rm10-3c95?k=RM10-3C95	3.54	1	3.54	
RM 12 cores (2 piece set)	RM12-3C95	https://www.digikey.com/en/products/filter/inductor/rm12-3c95?k=RM12-3C95	6.30	0	0	
RM 8 bobbin	B65912C15127001	https://www.digikey.com/en/products/filter/inductor/b65912c15127001?k=B65912C15127001	1.9	0	0	
RM 10 bobbin	B65819C15127001	https://www.digikey.com/en/products/filter/inductor/b65819c15127001?k=B65819C15127001	2.05	1	2.05	
RM 12 bobbin	B65819C15127001	https://www.digikey.com/en/products/filter/inductor/b65819c15127001?k=B65819C15127001	2.17	0	0	
RM 8 clamp	CLIP-RM8I	https://www.digikey.com/en/products/filter/inductor/clip-rm8i?k=CLIP-RM8I	0.31	0	0	
RM 10 clamp	CLIP-RM10I	https://www.digikey.com/en/products/filter/inductor/clip-rm10i?k=CLIP-RM10I	0.31	2	0.62	
RM 12 clamp	CLIP-RM12I	https://www.digikey.com/en/products/filter/inductor/clip-rm12i?k=CLIP-RM12I	0.49	0	0	
47 PARTS: CAPACITOR LIBRARY						
10 μF 100V 100μF	EL1V131HPS1016U	https://www.digikey.com/en/products/filter/capacitor/10uF-100V/1016uF/1016uF-100V?k=EL1V131HPS1016U	0.20	0	0	
47 μF 100V 100μF	ML2L14701V01020302	https://www.digikey.com/en/products/filter/capacitor/10uF-100V/1016uF/1016uF-100V?k=ML2L14701V01020302	0.83	3	2.49	
50 μF 22μF 35V X3R 0805	C2012X3R1V220M125A	https://www.digikey.com/en/products/filter/capacitor/c2012x3r1v220m125a?k=C2012X3R1V220M125A	0.82	4	3.28	
51 MLCC 4.7μF 35V X3R 0805	GRM21827VY475K7E15K	https://www.digikey.com/en/products/filter/capacitor/grm21827vy475k7e15k?k=GRM21827VY475K7E15K	0.3	0	0	
52 MLCC 10μF 35V X3R 1208	C3121X3R1V220M1604	https://www.digikey.com/en/products/filter/capacitor/c3121x3r1v220m1604?k=C3121X3R1V220M1604	0.97	0	0	
53 MLCC 10μF 35V X3R 1208	C1206X10K035T	https://www.digikey.com/en/products/filter/capacitor/c1206x10k035t?k=C1206X10K035T	0.44	0	0	
54 MLCC 10μF 35V X3R 0805	GRM21827VY475K7E15K	https://www.digikey.com/en/products/filter/capacitor/grm21827vy475k7e15k?k=GRM21827VY475K7E15K	0.34	4	1.36	
55 MLCC 10μF 35V X3R 1208	C1206X10K035T	https://www.digikey.com/en/products/filter/capacitor/c1206x10k035t?k=C1206X10K035T	0.30	4	1.20	
56 2.2 μF 25V Current sense decoupling 0603 50V	GRM19851V1250E121J	https://www.digikey.com/en/products/filter/capacitor/grm19851v1250e121j?k=GRM19851V1250E121J	0.21	3	0.63	
57 10 μF 25V Current sense decoupling for gate drive, LDO, I _q reg	GRM19851V1250E121J	https://www.digikey.com/en/products/filter/capacitor/grm19851v1250e121j?k=GRM19851V1250E121J	0.26	2	0.52	
58 1 μF 50V	D063X105K905CT	https://www.digikey.com/en/products/filter/capacitor/d063x105k905ct?k=D063X105K905CT	0.13	4	0.52	
59 1 μF 25V Current sense, op amp, regulator input	C0603X0250-104MN-CT	https://www.digikey.com/en/products/filter/capacitor/c0603x0250-104mn-ct?k=C0603X0250-104MN-CT	0.08	3	0.24	
60 LDO bypass	C0603X0250-331KNC-CT	https://www.digikey.com/en/products/filter/capacitor/c0603x0250-331knc-ct?k=C0603X0250-331KNC-CT	0.01	2	0.02	
61 Filter cap, 330 pF, 50V, NPO, 0805	C0603C0C0250-331KNC-CT	https://www.digikey.com/en/products/filter/capacitor/c0603c0c0250-331knc-ct?k=C0603C0C0250-331KNC-CT	0.01	2	0.02	
62 Current sense SHDN pin, 10pF, 5V, max 0603	C0603C0T0303-A07784	https://www.digikey.com/en/products/filter/capacitor/c0603c0t0303-a07784?k=C0603C0T0303-A07784	0.1	1	0.1	
63 PARTS: RESISTOR LIBRARY						
64 47 ohm, 0603, 1/4 W	73L2R47J	https://www.digikey.com/en/products/filter/resistor/73l2r47j?k=73L2R47J	0.31	0	0	
65 47 ohm, 0603, 1/4 W	A00630FR-7W1RL	https://www.digikey.com/en/products/filter/resistor/a00630fr-7w1rl?k=A00630FR-7W1RL	0.1	5	0.5	

Price: 54.78 \$